

# Latches and Flip-Flops

- Introduction to sequential logic
- Latches
  - SR Latch
  - Gated SR Latch
  - Gated D Latch
- Flip-Flops
  - JK Flip-flop
  - D Flip-flop
  - T Flip-flop
  - JK Master-Slave Flip-flop
  - Preset and Clear functions
  - 7474 and 7476 devices


# Flip-Flop

- Mostly used sequential circuit blocks for temporary storage (memory)
- For Flip-flops, output changes state only at a specified triggering input called clock (clk)
- For a latch, output changes state at a specified trigger level (high or low)

 
# Flip-Flop (cont.)

- D Latch vs D Flip Flop

Positive level triggered D Latch/  
Gated D Latch



Positive edge triggered D Flip-flop

 

Positive edge  
triggered


Symbol for "clk"

D	En	Q	$\bar{Q}$
0	1	0	1
1	1	1	<u>0</u>
x	0	Q	Q

D	clk	Q	$\bar{Q}$
0	↑	0	1
1	↑	1	0
x	↓	Q	$\bar{Q}$
x	0	Q	$\bar{Q}$
x	1	Q	$\bar{Q}$


# Flip-Flop (cont.)

Negative level triggered D Latch

 

D	En	Q	$\bar{Q}$
0	0	0	1
1	0	1	0
x	1	Q	$\bar{Q}$

Negative edge triggered D Flip-flop

 


Negative edge  
triggered

D	clk	Q	$\bar{Q}$
0	↓	0	1
1	↓	1	0
x	↑	Q	$\bar{Q}$
x	0	Q	$\bar{Q}$
x	1	Q	$\bar{Q}$

 
# Flip-flop (cont.)

- Draw the output waveform for the positive and negative edge triggered D flip-flops


 
# Flip-Flop (cont.)

- How to design flip-flops?
- Recall the Gated D Latch




For Gated D Latch,  
 $Q \leq D$  when  $En = 1$

For D Flip-flop,  
 $Q \leq D$  when  $En = \uparrow$


We need a pulse transition detector for a D Flip-flop, in order  
To detect  $\uparrow$

# Flip-Flop (cont.)

- Pulse transition detector

 


Circuit diagram

 


Waveform

Pulse transition detector

 

Block diagram


# D Flip-flop

 

A positive edge of clk results in a short pulse at output of PTD, therefore, causes  $Q \leq D$  only at that instant (pulse duration)  
Q is maintained until the next positive edge of clk


# SR Flip-flop

- Recall the problem with SR Flip-flop

 

When  $S = 1$  and  $R = 1$ , the outputs  $Q$  and  $\bar{Q}$  equal to 1  
 To overcome this problem,  $Q$  and  $\bar{Q}$  is fed back to the Gated NANDs  
 which now becomes the JK Flip-flop  
 $S_x$  and  $R_x$  can never be equal to 0 at same time

# JK Flip-flop

 

J	K	clk	Q	$\bar{Q}$
0	0	$\uparrow$	Q	$\bar{Q}$
0	1	$\uparrow$	0	1
1	0	$\uparrow$	1	0
1	1	$\uparrow$	$\bar{Q}$	Q
x	x	-	Q	$\bar{Q}$

When  $J = 1$  and  $K = 1$ ,  $Q$  and  $\bar{Q}$  toggles


When  $J = 0$  and  $K = 0$ ,  $Q$  and  $\bar{Q}$  maintains

When  $J = 0$  and  $K = 1$ ,  $Q = 0$  (Reset)

When  $J = 1$  and  $K = 0$ ,  $Q = 1$  (Set)
 
# D Flip-flop

- We can also construct a D Flip-flop from JK Flip-flop by shorting J and K with an inverter




D	clk	Q	$\bar{Q}$
0	$\uparrow$	0	1
1	$\uparrow$	1	0
x	-	Q	$\bar{Q}$

$Q \leq D$  when  $clk = \uparrow$   
 Else  $Q \leq Q$
 
# T Flip-flop

- Another type of flip-flop, the T Flip-flop can be constructed from the JK flip flop by shorting J and K inputs




T	clk	Q	$\bar{Q}$
0	$\uparrow$	Q	$\bar{Q}$
1	$\uparrow$	$\bar{Q}$	Q
X	-	Q	$\bar{Q}$


$Q \leq \bar{Q}$  when  $T = 1$  and  $clk = \uparrow$   
 Else  $Q \leq Q$
 
# T Flip-flop (cont.)

- Draw the output waveform for the positive edge triggered T Flip-flop




# JK Master Slave Flip-Flop

 

Master latches data at positive edge of clk  
 Slave latches data at negative edge of clk  
 $Q_{ms}$  is therefore valid on the negative edge of clk
 
# JK Master Slave Flip-flop (cont.)

- Draw the output for JK Flip-flop and the JK Master Slave Flip-flop (MS-JK)




Q (JK Flip-flop)

Q (MS-JK Flip-flop)
 
# Flip-flop Extra Features


- Positive edge triggered D Flip-flop with active high Input Enable



If  $En = 1$   
 $Q \leq D$  when  $clk = \uparrow$   
Else  
 $Q \leq Q$

 
# Flip-flop Extra Features (cont.)

- Positive Edge Triggered D Flip-flop with active low clear and active low preset functions


 
# Flip-flop Extra Features (cont.)

- Putting all together – Positive Edge Triggered D Flip-flop with active high enable, active low preset and active low clear



What is the input condition that  $Q \leq D$ ?  
 $En = 1, clk = \uparrow, CLR = 1, PRE = 1$

How to force  $Q \leq 1$ ?  
 $En = x, clk = x, CLR = 1, PRE = 0$

How to force  $Q \leq 0$ ?  
 $En = x, clk = x, CLR = 0, PRE = 1$

How to set  $Q \leq Q$  at positive edge of clk?  
 $En = 0, clk = \uparrow, CLR = 1, PRE = 1$

# Flip-flop IC

- The 7474 Dual Positive Edge Triggered D Flip-flop with preset, clear, and complementary outputs
- The 7476 Dual Master-Slave JK Flip-flops with clear, preset and complementary outputs